

TOBB University of Economics and Technology

Department of Electrical and Electronics Engineering

ELE 224L – Electronic Circuits Laboratory

Experiment 5 – Preliminary Work: BJT Amplifiers

Name Surname	Beşir Kerem Üstüntürk
Student ID	251201037
Date	October 11, 2026

1 INTRODUCTION

1.1 Objective of the Experiment

The objective of this experiment is to learn the operating principles of the common-emitter and the common-collector amplifiers, which are two of the three basic BJT amplifier configurations. For both circuits, the DC operating point, the small-signal voltage gain, the input and output resistances and the maximum output voltage swing are calculated and compared with SPICE simulations. The wiring of the circuits on a breadboard is also studied, including the detection of the errors in a given drawing.

1.2 Benefits of the Experiment

The experiment shows how a BJT amplifier is analysed in two steps (DC bias, then AC small signal), how the emitter bypass capacitor changes the gain by a factor of about 80, why the emitter follower has a gain close to but never above one, and how the exponential characteristic of the BJT limits the undistorted output amplitude. It also trains the checking of the capacitor impedances at the test frequency, the use of a THD criterion for distortion, and the reading and correcting of a breadboard drawing. These skills are required in all analog design work.

2 CALCULATIONS AND SIMULATIONS

2.1 BJT Amplifier Circuit Diagram and Breadboard

The parameters of the BC238A were taken from the datasheet (Fairchild BC237/238/239): $\beta = 170$ (the average of the class A range of 120–220) and $V_{BE(on)} = 0.62$ V (typical value at $I_C = 2$ mA, $V_{CE} = 5$ V). The Early voltage is neglected. These values are used in all calculations of this section.

Table 2.1.1 BJT parameters used in the calculations

Parameter	Value
β (average)	170
$V_{BE(on)}$ (typical)	0.62 V

The connections of the given breadboard drawing (Figure 2.1.1) were read hole by hole, and the electrical nodes were extracted automatically and compared with the circuit diagram of the common-emitter amplifier (Figure 2.1.2). The comparison showed the four wiring errors and one missing element that are listed in Table 2.1.2 and marked in Figure 2.1.1. The values of

the resistors read from the colour codes (5.6 kΩ, 120 kΩ, 1.8 kΩ, 39 kΩ, 15 kΩ) and the connections of the transistor (*C* on column 18, *B* on 19, *E* on 20) are correct.

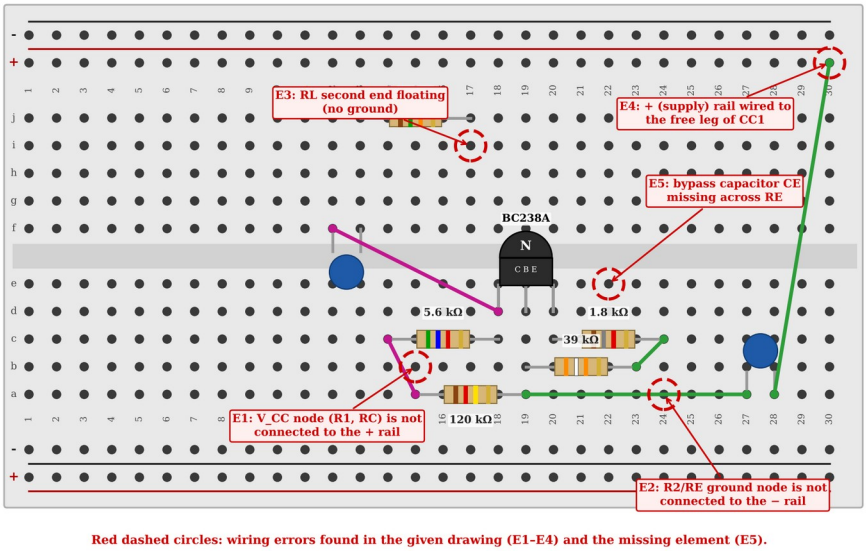


Figure 2.1.1 The given breadboard drawing of the common-emitter amplifier; the errors are marked with red dashed circles.

Table 2.1.2 Errors found in the given breadboard drawing and their corrections

No.	Error	Correction
E1	The node where R_1 and R_C meet (columns 14–15) is not connected to the + rail.	No supply voltage reaches the circuit; V_{CC} must be wired to this node (red wire from the + rail to column 15).
E2	The node where R_2 and R_E meet (columns 23–24) is not connected to the − rail.	The circuit has no ground reference; a wire from this node to the − (GND) rail is required.
E3	The second leg of R_L (column 17, upper block) is not connected to anything.	The load is not grounded, so C_{C2} and R_L do not form a path to ground; R_L must be wired to the GND rail.
E4	The + (supply) rail is wired to the free leg of C_{C1} (column 28).	The input coupling capacitor would be tied to the supply instead of the signal source; this wire must be removed and the function-generator output connected to C_{C1} (v_i).
E5	The emitter bypass capacitor C_E is missing.	C_E (22 nF) must be connected in parallel with R_E (between the emitter column and the ground node).

The corrected drawing is shown in Figure 2.1.3. The names and values of the circuit elements are given in Table 2.1.3; the missing element is the bypass capacitor C_E (drawn in red). The correctness of the corrected drawing was checked by the same automatic node extraction: the node lists of the drawing and of the circuit diagram are identical.

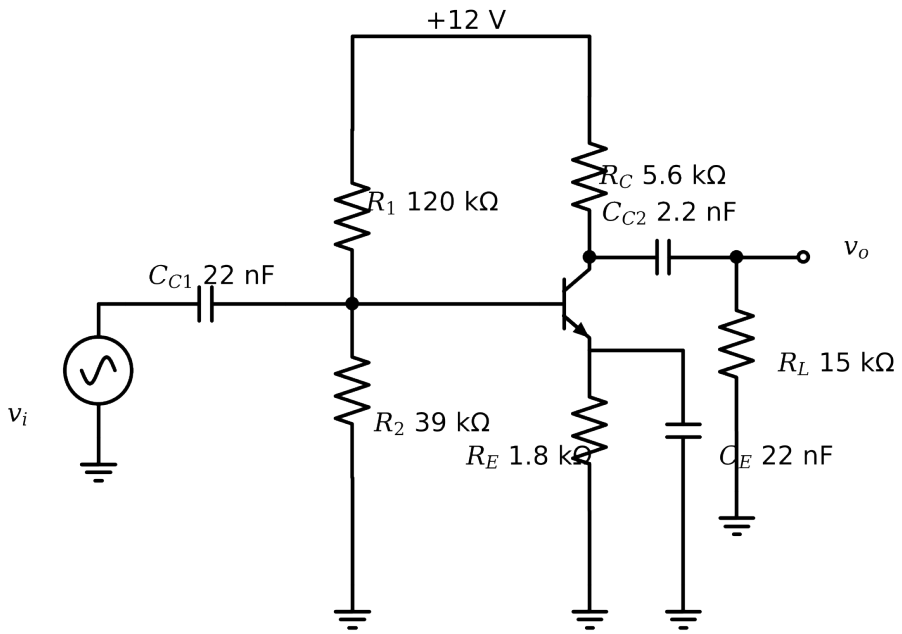


Figure 2.1.2 Common-emitter amplifier circuit diagram.

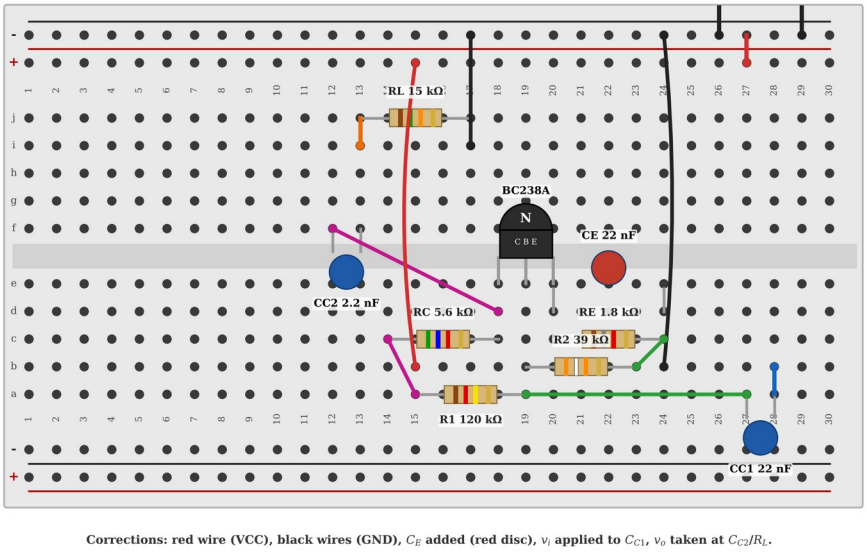


Figure 2.1.3 Corrected breadboard drawing of the common-emitter amplifier (with C_E added).

Table 2.1.3 Names and values of the circuit elements of the common-emitter amplifier

Name	Value	Function
Q1	BC238A (NPN)	Amplifying element
R1	120 kΩ	Upper bias resistor (+V_{CC} to base)
R2	39 kΩ	Lower bias resistor (base to GND)
RC	5.6 kΩ	Collector resistor
RE	1.8 kΩ	Emitter resistor (DC stabilisation)
RL	15 kΩ	Load resistor
CC1	22 nF	Input coupling capacitor
CC2	2.2 nF	Output coupling capacitor
CE	22 nF (missing)	Emitter bypass capacitor

The common-collector amplifier of the experiment sheet (Figure 2.1.4) was drawn on the breadboard as shown in Figure 2.1.5. The collector is wired directly to the + rail (there is no collector resistor), R_1 and R_2 form the base divider, the output is taken from the emitter through C_{C2} and loaded by R_L, and the input is applied to the base through C_{C1}. The connections were verified automatically against the circuit diagram.

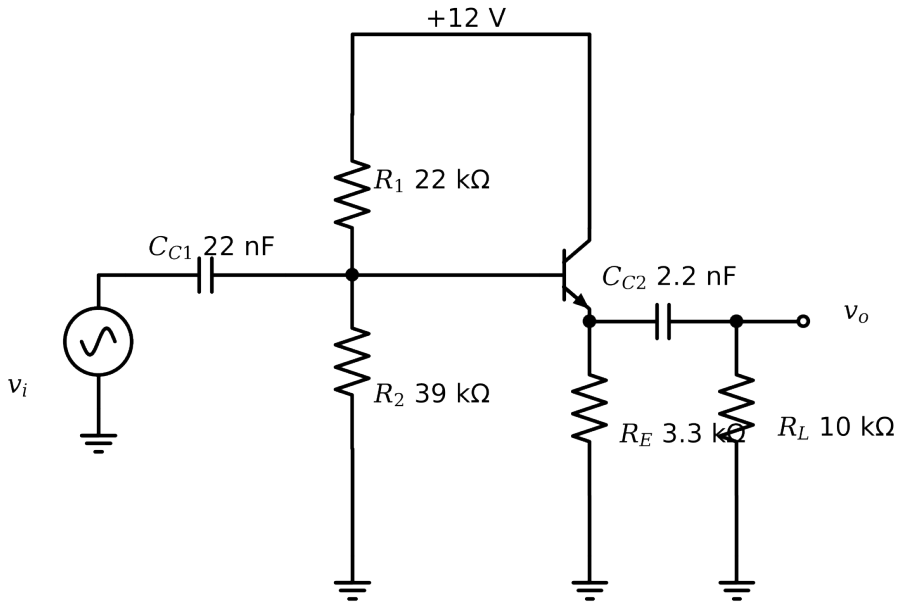


Figure 2.1.4 Common-collector amplifier circuit diagram.

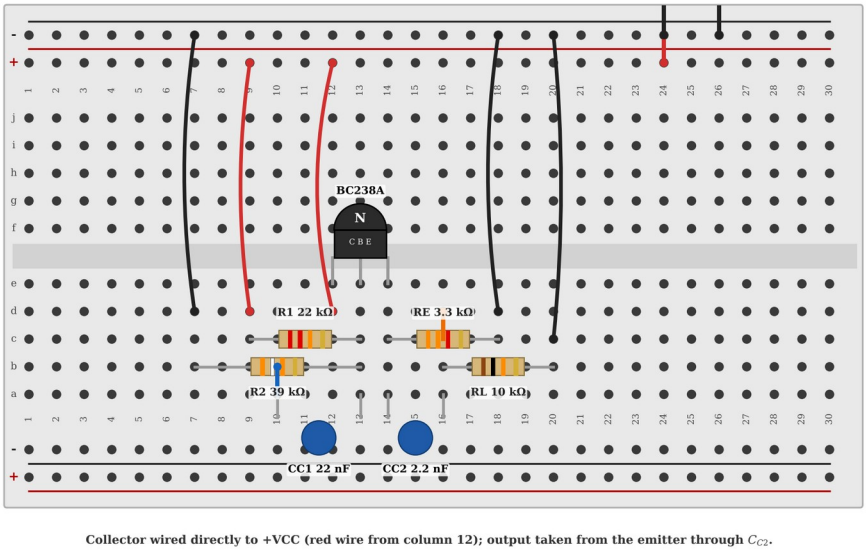


Figure 2.1.5 Common-collector amplifier on the breadboard.

2.2 Common-Emitter Amplifier Analysis

DC analysis. The capacitors are open circuits. The base divider is replaced by its Thévenin equivalent, $V_{TH} = V_{CC} R_2 / (R_1 + R_2) = 2.943$ V and $R_{TH} = R_1 \parallel R_2 = 29.43$ kΩ, and the base loop gives (2.1).

$$I_B = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (\beta + 1) R_E} = \frac{2.9434 - 0.62}{29.434\,\text{k}\Omega + 171 \cdot 1.8\,\text{k}\Omega} = 6.890\,\mu\text{A} \tag{2.1}$$

Then $I_C = \beta I_B = 1.171$ mA, $I_E = (\beta + 1) I_B = 1.178$ mA, and $V_{CE} = V_{CC} - I_C R_C - I_E R_E = 12 - 1.171 \times 5.6 - 1.178 \times 1.8 = 3.321$ V. Since $V_{CE} > 0.2$ V, the transistor is in the active region. The small-signal parameters are $g_m = I_C / V_T = 45.05$ mS, $r_\pi = \beta / g_m = 3.774$ kΩ and $r_e = V_T / I_E = 22.07\,\Omega$ (with $V_T = 26$ mV).

AC analysis (mid-band). The coupling and bypass capacitors are short circuits and V_{CC} is an AC ground. With C_E, the emitter is grounded and the gain is given by (2.2); without C_E, the emitter resistor produces negative feedback and the gain is given by (2.3), where $R_L' = R_C \parallel R_L = 4.078$ kΩ. The output resistance (looking into the collector, R_L excluded) is $R_o = R_C = 5.6$ kΩ, and the input resistance is given by (2.4).

$$A_V = -g_m R_L' = -45.05\,\text{mS} \times 4.078\,\text{k}\Omega = -183.7 \tag{2.2}$$

$$A_V = -\frac{\beta R_L'}{r_\pi + (\beta + 1) R_E} = -\frac{170 \times 4.078\,\text{k}\Omega}{3.774\,\text{k}\Omega + 171 \times 1.8\,\text{k}\Omega} = -2.225 \tag{2.3}$$

$$R_i = R_1 \parallel R_2 \parallel r_\pi = 3.34\,\text{k}\Omega\,(\text{with } C_E),\ R_i = R_1 \parallel R_2 \parallel \left[r_\pi + (\beta + 1) R_E\right] = 26.89 \tag{2.4}$$

Maximum output swing. The AC load line passes through the Q point with the slope $-1/R_L'$. With C_E, the collector voltage can increase by $I_{CQ} R_L' = 4.776$ V before the transistor is cut off and decrease by $V_{CEQ} - V_{CE(sat)} = 3.121$ V before it saturates, so that the symmetrical swing is limited by saturation: $V_{O,pp,max} = 2 \times 3.121 = 6.241$ V. Without C_E, the AC load seen by the emitter–collector path is $R_L' + R_E$, the collector current can decrease by I_{CQ} or increase by $(V_{CEQ} - 0.2)/(R_L' + R_E) = 0.5309$ mA, and the output swing is $V_{O,pp,max} = 2 \times 0.5309\,\text{mA} \times R_L' = 4.330$ V.

Table 2.2.1 Calculated values for the common-emitter amplifier circuit (the last two rows are additional)

	With C_E	**Without C_E**
V_{BEQ} (V)	0.62	0.62
V_{CEQ} (V)	3.321	3.321
I_{BQ} (mA)	0.006890	0.006890
I_{CQ} (mA)	1.171	1.171
$A_V = V_o / V_i$ (mid-band)	−183.7	−2.225
V_O (peak-to-peak, max.) (V)	6.241	4.330
R_i (kΩ) / R_o (kΩ)	3.34 / 5.6	26.9 / 5.6
$\lvert A_V \rangle$ at 100 kHz (phasor analysis)	52.74	2.223

The mid-band gain assumes that C_E is a perfect short circuit. At the test frequency of 100 kHz, the impedance of $C_E = 22$ nF is $1/(2\pi f C_E) = 72\,\Omega$, which is larger than $r_e = 22.1\,\Omega$. The gain is then reduced to $\lvert A_V \rangle \approx R_L' / (r_e + \lvert Z_E \rangle)$, and a complete phasor analysis (including C_{C1}, C_{C2} and C_E) gives $\lvert A_V \rangle = 52.7$ at 100 kHz instead of 184. A bypass capacitor of about 0.16 µF would be needed for 90% of the mid-band gain at 100 kHz. Without C_E, the gain is independent of frequency in this range (2.22).

SPICE. The circuit was built with the BC238A model (Appendix A). The DC and AC results are compared with the calculations in Table 2.2.2, the frequency response is shown in Figure 2.2.1. A sinusoidal input of 100 kHz with zero offset was applied, and the output was analysed with the total harmonic distortion (THD) obtained from the FFT of ten steady-state periods. The THD of the output as a function of the input amplitude is shown in Figure 2.2.4. An output waveform is called undistorted when THD $\leq 1\%$ (a THD of 5% is also given for reference), since the visual detection of the distortion of a sine wave is possible only above about 5%.

Table 2.2.2 Comparison of the calculation and SPICE for the common-emitter amplifier (Error = (SPICE − calculation)/calculation)

Quantity	Calculation	SPICE	Error
V_{BEQ} (V)	0.62	0.6066	-2.2%
V_{CEQ} (V)	3.321	3.270	-1.5%
I_{BQ} (µA)	6.890	6.929	+0.6%
I_{CQ} (mA)	1.171	1.178	+0.6%
$\lvert A_V \rvert$ at 100 kHz, with C_E	52.74	52.75	+0.0%
$\lvert A_V \rvert$ at 100 kHz, without C_E	2.223	2.223	-0.0%
$\lvert A_V \rvert$ maximum of the curve, with C_E (SPICE, at 1585 kHz)	183.7	177.5	-3.3%
$\lvert A_V \rvert$ mid-band, without C_E	2.225	2.201	-1.1%
R_i at 100 kHz, with C_E (kΩ)	10.72	9.879	-7.8%
R_i at 100 kHz, without C_E (kΩ)	26.89	26.65	-0.9%

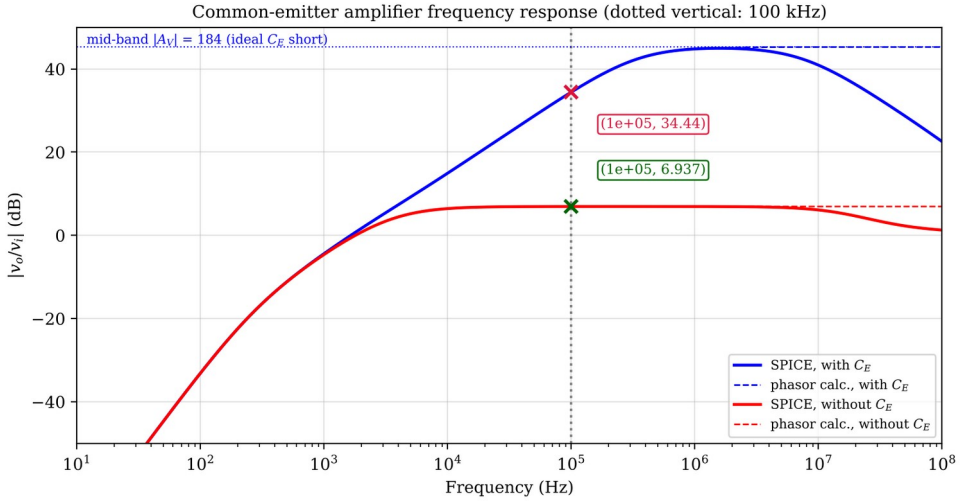


Figure 2.2.1 Frequency response of the common-emitter amplifier (SPICE and phasor calculation).

Table 2.2.3 Coordinates of the cursors in Figure 2.2.1

Cursor	x coordinate	y coordinate
X1	Frequency = 1.000e+05 Hz	$\lvert v_o/v_i \rvert$ = 34.44 dB
X2	Frequency = 1.000e+05 Hz	$\lvert v_o/v_i \rvert$ = 6.937 dB

The simulation was repeated in LTspice; the waveform window with the cursors is shown in Figure 2.2.2, and the cursor readings are compared with the ngspice values at the same x in Table 2.2.4. The agreement shows that the result does not depend on the simulator.

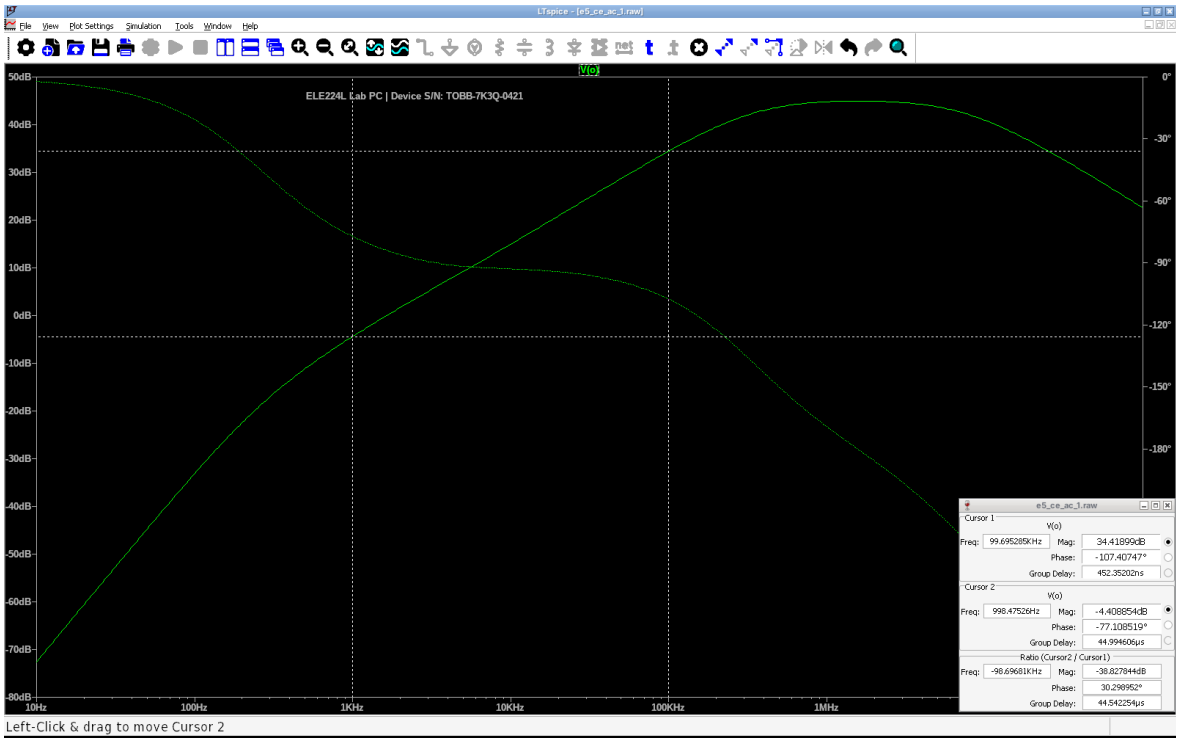


Figure 2.2.2 LTspice AC analysis of the common-emitter amplifier with the emitter bypass capacitor C_E (device serial number: TOBB-7K3Q-0421)

Table 2.2.4 Cursor coordinates read in Figure 2.2.2 and the ngspice values at the same x

Cursor	x coordinate	Quantity	LTspice	ngspice	Difference
1	f = 99.695 kHz	$\lvert V_O \rvert$	34.419 dB	34.42 dB	-0.001 dB
1	f = 99.695 kHz	$\angle V_O$	−107.41 °	−107.39 °	-0.022 °
2	f = 998.48 Hz	$\lvert V_O \rvert$	−4.4089 dB	−4.409 dB	+0.000 dB
2	f = 998.48 Hz	$\angle V_O$	−77.109 °	−77.108 °	-0.001 °

The LTspice result for this case is shown in Figure 2.2.3 and the cursor comparison is given in Table 2.2.5.

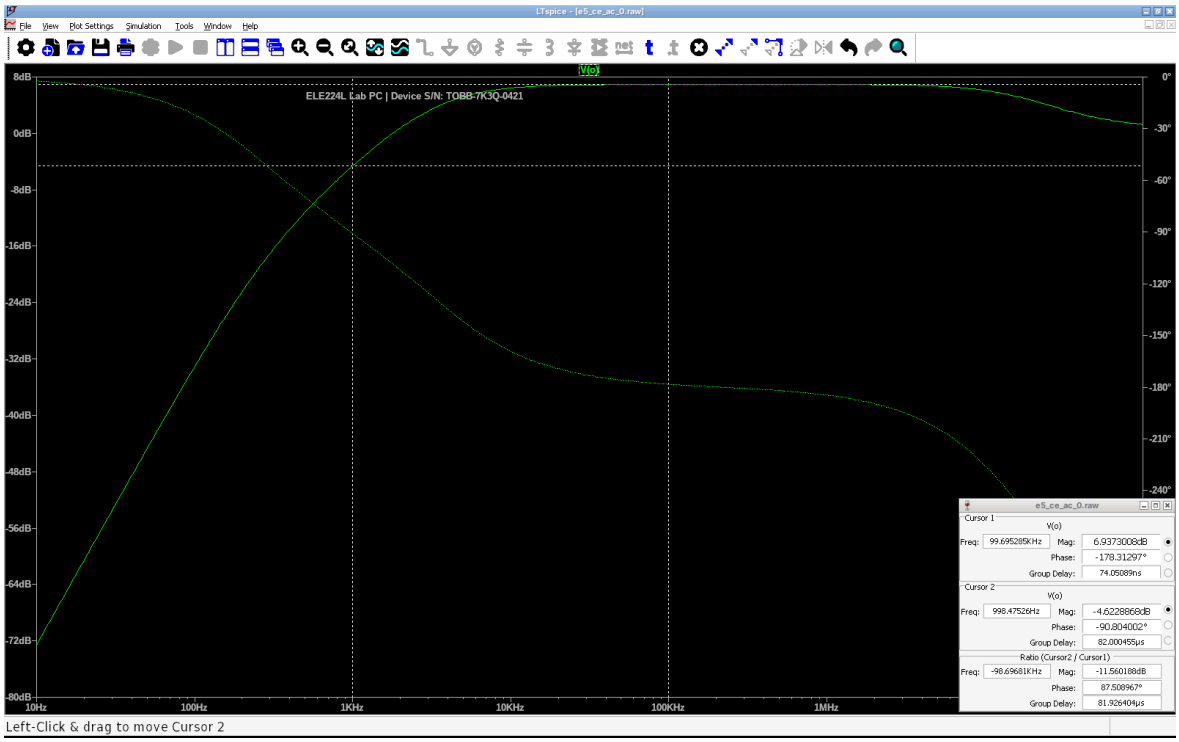


Figure 2.2.3 LTspice AC analysis of the common-emitter amplifier without C_E (device serial number: TOBB-7K3Q-0421)

Table 2.2.5 Cursor coordinates read in Figure 2.2.3 and the ngspice values at the same x

Cursor	x coordinate	Quantity	LTspice	ngspice	Difference
1	f = 99.695 kHz	$\lvert V_O \rvert$	6.9373 dB	6.9374 dB	-0.000 dB
1	f = 99.695 kHz	$\angle V_O$	−178.31 °	−178.31 °	-0.000 °
2	f = 998.48 Hz	$\lvert V_O \rvert$	−4.6229 dB	−4.623 dB	+0.000 dB
2	f = 998.48 Hz	$\angle V_O$	−90.804 °	−90.803 °	-0.001 °

Highest undistorted amplitude. For the circuit with C_E, the THD reaches 1% at an input amplitude of 7.24 mV peak (14.5 mV peak-to-peak), at which the output is 0.764 V peak-to-peak (gain 52.7, equal to the phasor result); the THD reaches 5% at 69.5 mV peak-to-peak. For the circuit without C_E, the THD reaches 1% at 2.11 V peak-to-peak input (4.66 V peak-to-peak output) and 5% at 3.37 V peak-to-peak. The corresponding waveforms are shown in Figure 2.2.5 (with C_E) and Figure 2.2.6 (without C_E); the top panel of each figure shows the highest undistorted amplitude, and the other panels show a larger amplitude and an overdriven input.

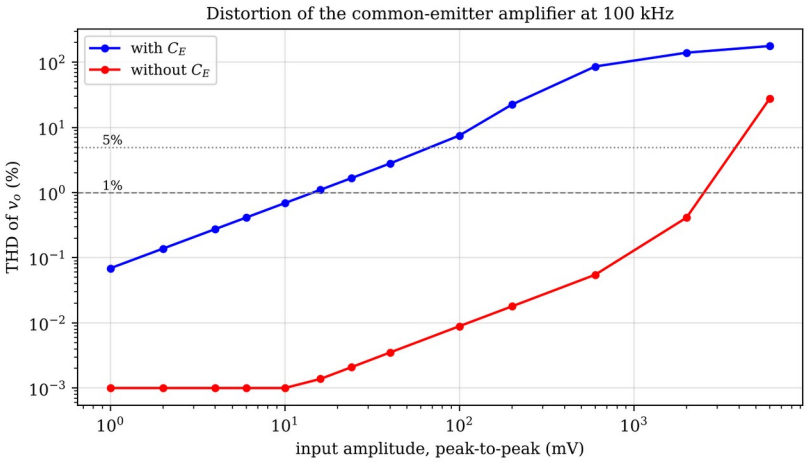


Figure 2.2.4 Total harmonic distortion of the output voltage versus input amplitude (SPICE, 100 kHz).

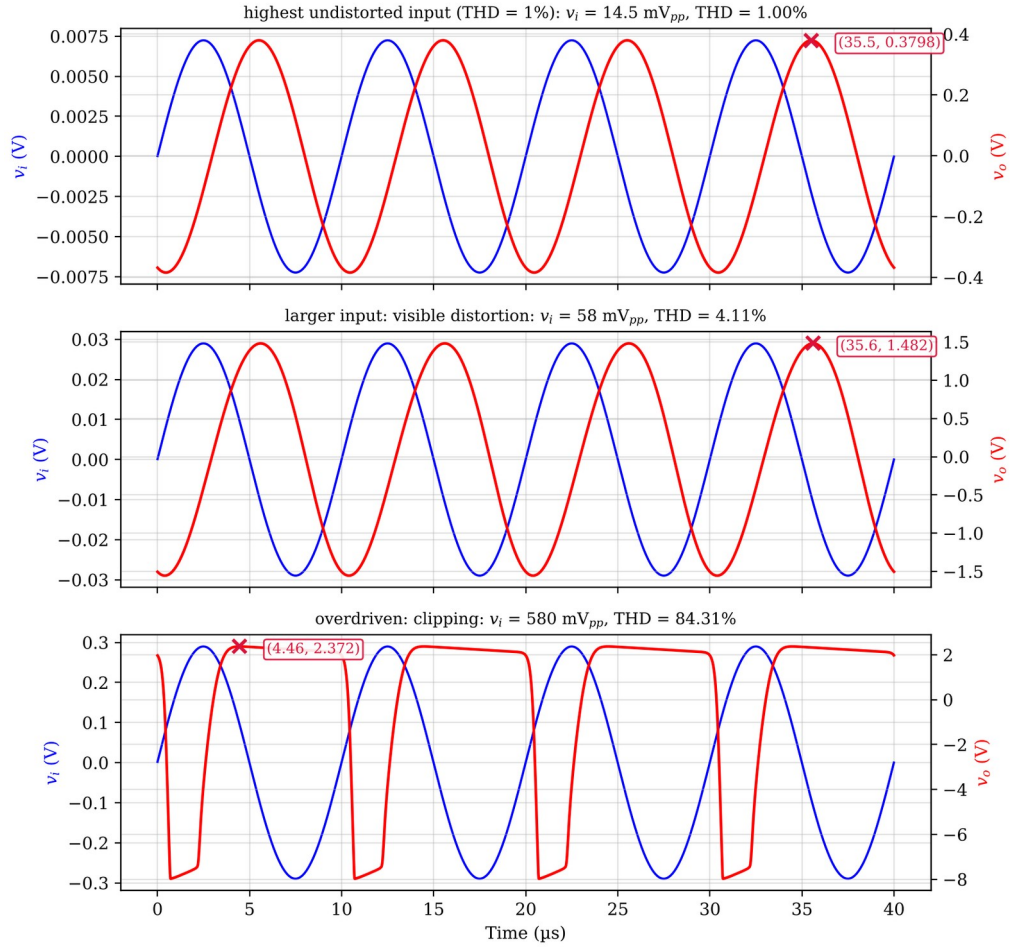


Figure 2.2.5 Input and output voltages of the circuit with C_E at three input amplitudes (the output waveform is shown with its DC level removed).

Table 2.2.6 Coordinates of the cursors in Figure 2.2.5

Cursor	x coordinate	y coordinate
X1	= 35.50	v_o = 0.3798 V
X2	= 35.60	v_o = 1.482 V
X3	= 4.460	v_o = 2.372 V

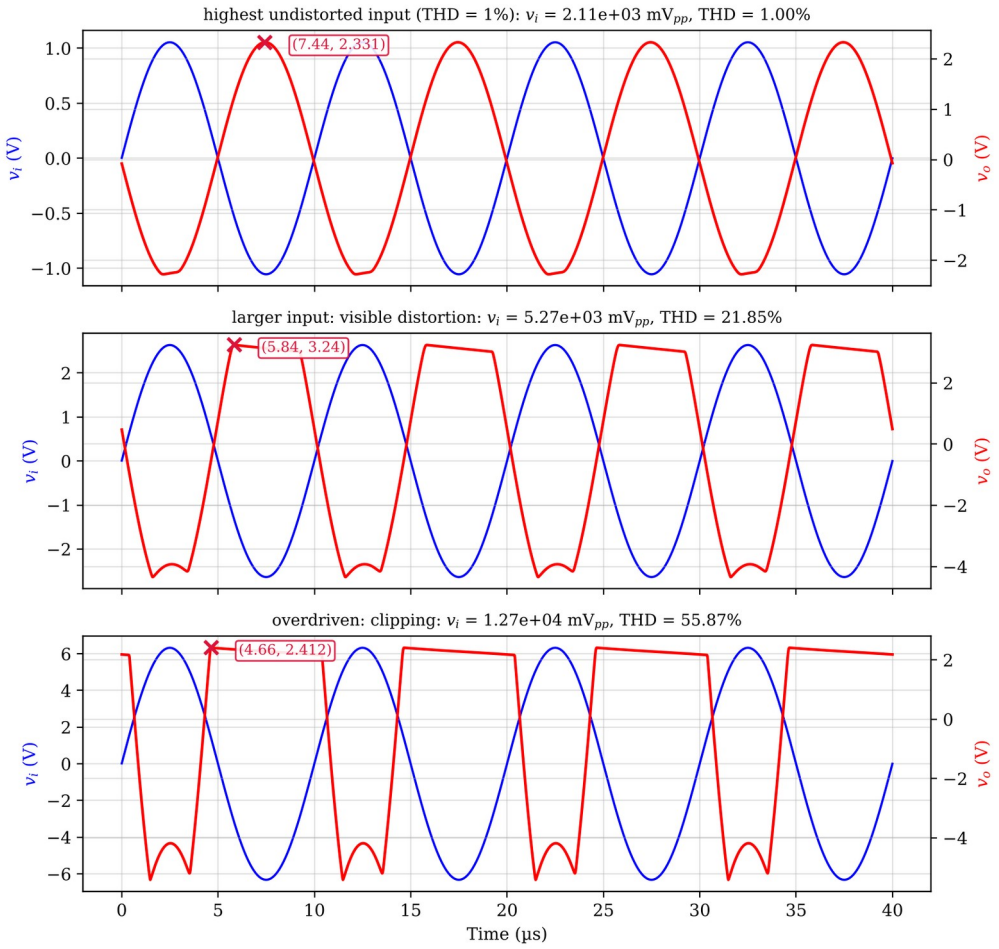


Figure 2.2.6 Input and output voltages of the circuit without C_E at three input amplitudes.

Table 2.2.7 Coordinates of the cursors in Figure 2.2.6

Cursor	x coordinate	y coordinate
X1	= 7.440	v_o = 2.331 V
X2	= 5.840	v_o = 3.240 V
X3	= 4.660	v_o = 2.412 V

The limits above are very different from the load-line limits of Table 2.2.1 (6.24 V and 4.33 V peak-to-peak). With C_E, the output is limited by the curvature of the exponential I_C–V_{BE} characteristic, long before clipping: the second harmonic is approximately $v_{be}/(4\,V_T)$ of the fundamental for a bypassed emitter, so that a base–emitter signal of only a few millivolts already gives about 1% distortion. Without C_E, the emitter resistor linearizes the stage (the base–emitter signal is only a small fraction of v_i), so that the distortion starts only when the signal approaches the clipping level, at about the load-line value. When the input is increased

much more, the output clips (with the coupling capacitor shifting the DC level, the clipped output swings 10.7 V peak-to-peak with C_E and 7.82 V without C_E).

2.3 Common-Collector Amplifier Analysis

DC analysis. With $V_{TH} = 12 \times 39/61 = 7.672$ V and $R_{TH} = 14.07$ kΩ, (2.5) gives the base current, and $V_{CE} = V_{CC} - I_E R_E$ because the collector is connected to V_{CC}.

$$I_B = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (\beta + 1) R_E} = \frac{7.6721 - 0.62}{14.066\,\text{k}\Omega + 171 \cdot 3.3\,\text{k}\Omega} = 12.193\,\mu\text{A} \tag{2.5}$$

Then $I_C = 2.073$ mA, $I_E = 2.085$ mA, and $V_{CE} = 12 - 2.085 \times 3.3 = 5.119$ V (active region). The small-signal parameters are $g_m = 79.72$ mS, $r_\pi = 2.132$ kΩ and $r_e = 12.5\,\Omega$.

AC analysis. The AC load of the emitter is $R_E' = R_E \parallel R_L = 2.481$ kΩ. The voltage gain, the input resistance and the output resistance (with an ideal source) are given by (2.6)–(2.8). The maximum symmetrical swing is limited by saturation on the positive side ($V_{CEQ} - 0.2 = 4.919$ V) and by cut-off on the negative side ($I_{EQ} R_E' = 5.173$ V), and $V_{O,pp,max} = 2 \times 4.919 = 9.839$ V.

$$A_V = \frac{(\beta + 1) R_E'}{r_\pi + (\beta + 1) R_E'} = \frac{171 \times 2.481\,\text{k}\Omega}{2.132\,\text{k}\Omega + 171 \times 2.481\,\text{k}\Omega} = 0.9950 \tag{2.6}$$

$$R_i = R_1 \parallel R_2 \parallel \left[r_\pi + (\beta + 1) R_E' \right] = 13.62\,\text{k}\Omega \tag{2.7}$$

$$R_o = R_E \parallel \frac{r_\pi}{\beta + 1} = 12.42\,\Omega \tag{2.8}$$

Table 2.3.1 Calculated values for the common-collector amplifier circuit

	Calculated value
V_{BEQ} (V)	0.62
V_{CEQ} (V)	5.119
I_{BQ} (mA)	0.01219
I_{CQ} (mA)	2.073
$A_V = V_o / V_i$	0.9950
V_O (peak-to-peak, max.) (V)	9.839
R_i (kΩ) / R_o (Ω) (additional)	13.6 / 12.4

Table 2.3.2 Comparison of the calculation and SPICE for the common-collector amplifier

Quantity	Calculation	SPICE	Error
V_{BEQ} (V)	0.62	0.6213	+0.2%
V_{CEQ} (V)	5.119	5.121	+0.0%
I_{BQ} (μA)	12.19	12.19	-0.0%
I_{EQ} (mA)	2.085	2.085	-0.0%
A_V at 100 kHz	0.9924	0.9923	-0.0%
R_i at 100 kHz (kΩ)	13.62	13.62	-0.0%
R_o at 100 kHz (Ω)	12.42	12.57	+1.2%

The input and output voltage graphs of the common-collector amplifier (1 V peak, 100 kHz) are shown in Figure 2.3.1, and the frequency response is shown in Figure 2.3.2. The output follows the input with a gain of 0.9923 and without a phase shift (THD = 0.024%). The DC level of the output is removed by C_{C2}, and the transistor stays in the active region. When the input is increased to 8 V peak (Figure 2.3.4), the output clips at +6.57 V and −4.44 V (peak-to-peak 11.0 V), which is larger than the symmetrical load-line value of 9.84 V, because at large signals the base-current peaks charge C_{C1} and shift the bias point to a larger swing.

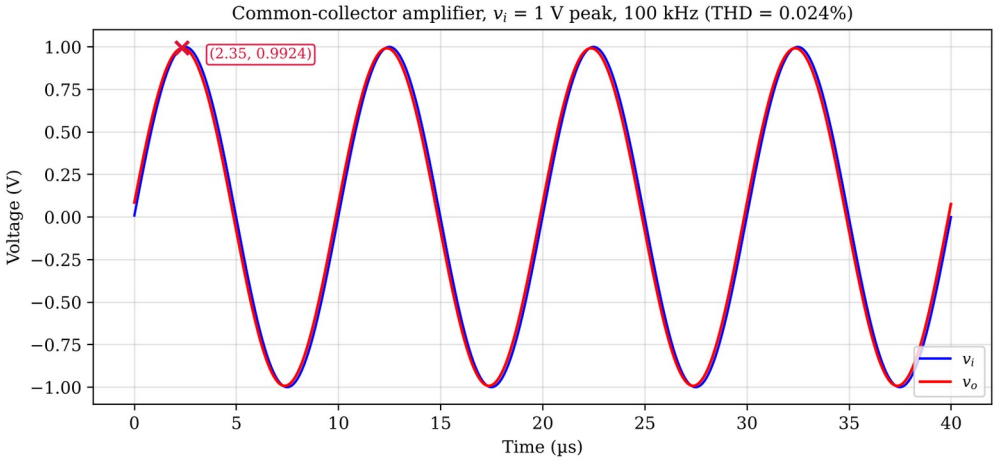


Figure 2.3.1 Input and output voltages of the common-collector amplifier (ngspice).

Table 2.3.3 Coordinates of the cursors in Figure 2.3.1

Cursor	x coordinate	y coordinate
X1	Time = 2.350 μs	Voltage = 0.9924 V

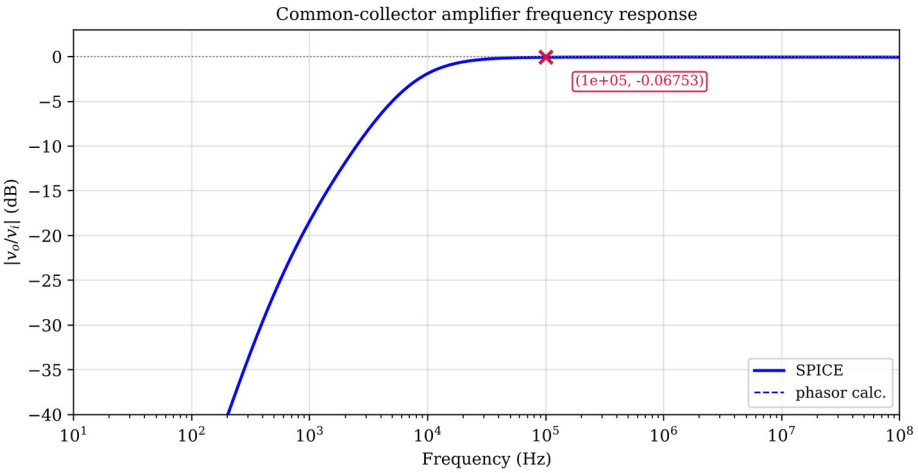


Figure 2.3.2 Frequency response of the common-collector amplifier.

Table 2.3.4 Coordinates of the cursors in Figure 2.3.2

Cursor	x coordinate	y coordinate
X1	Frequency = 1.000e+05 Hz	$\left\|v_o/v_i\right\|$ = −0.06753 dB

The LTspice result for this case is shown in Figure 2.3.3 and the cursor comparison is given in Table 2.3.5.

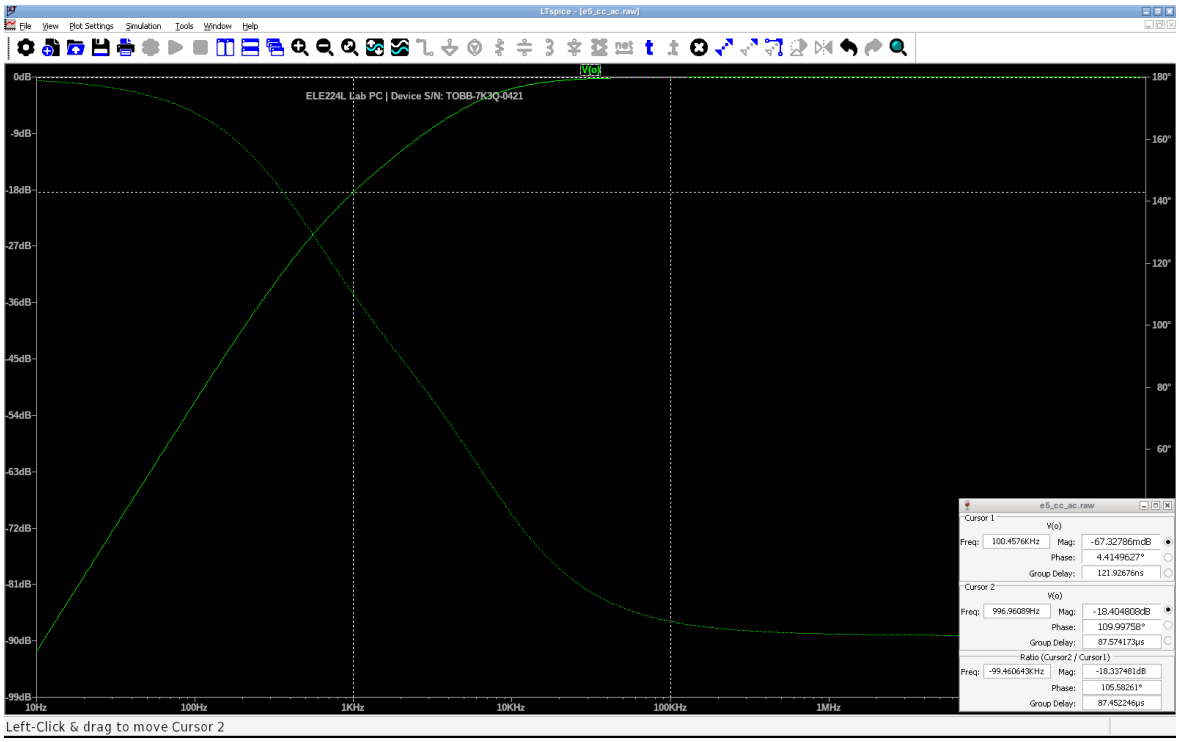


Figure 2.3.3 LTspice AC analysis of the common-collector (emitter-follower) amplifier (device serial number: TOBB-7K3Q-0421)

Table 2.3.5 Cursor coordinates read in Figure 2.3.3 and the ngspice values at the same x

Cursor	x coordinate	Quantity	LTspice	ngspice	Difference
1	f = 100.458 kHz	$\lvert V_O \rvert$	−0.067328 dB	−0.067329 dB	+0.000 dB
1	f = 100.458 kHz	$\angle V_O$	4.415 °	4.4153 °	-0.000 °
2	f = 996.96 Hz	$\lvert V_O \rvert$	−18.405 dB	−18.405 dB	+0.001 dB
2	f = 996.96 Hz	$\angle V_O$	110 °	110 °	-0.002 °

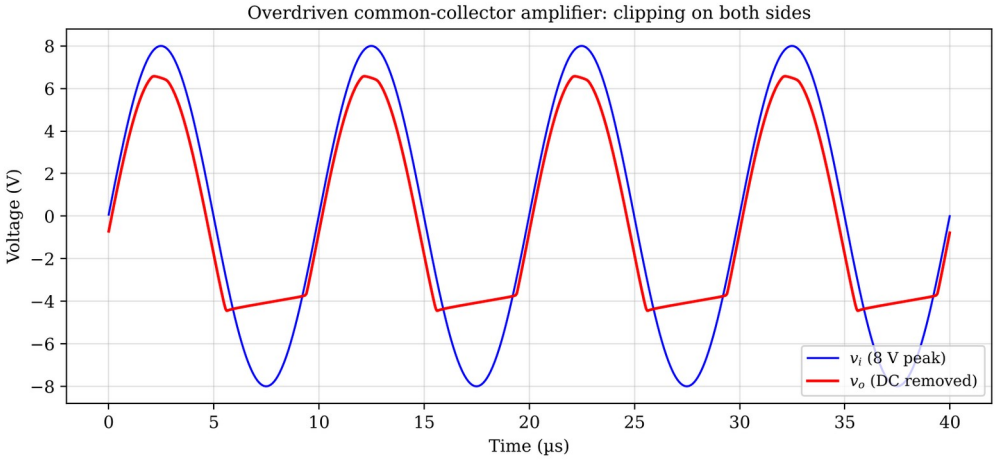


Figure 2.3.4 Overdriven common-collector amplifier (the output clips on both sides).

Is it possible to double the gain? No. From (2.6), $A_V = \dfrac{(\beta+1)R_E'}{r_\pi + (\beta+1)R_E'}$ is smaller than one for any finite β, because the denominator is larger than the numerator by r_π. The gain approaches one only when $(\beta+1)R_E' \gg r_\pi$ (equivalently $R_E' \gg r_e$), and it is already 0.9950. The largest possible improvement is therefore 0.5%, and a gain of about 2 cannot be obtained by changing the resistors or the bias. Physically, the output follows $v_e = v_b - V_{BE}$ with V_{BE} almost constant, so that the emitter follower provides current gain ($\beta+1$) and impedance transformation, but not voltage gain. A voltage gain of 2 requires another configuration (for example, a common-emitter stage) or an additional gain stage.

2.4 Maximum Voltage Swing (Extra Points)

The voltage swing of the common-collector amplifier is limited by two boundaries of the AC load line: the saturation limit on the positive side, $V_{CEQ} - V_{CE(sat)}$, and the cut-off limit on the negative side, $I_{EQ}R_E'$. The largest symmetrical swing is obtained when the two limits are equal, i.e., when $V_{CEQ} = I_{EQ}R_E'$ with $V_{CEQ} = V_{CC} - I_{EQ}R_E$, which gives the optimum emitter current of (2.9).

$$I_{EQ,opt}=\frac{V_{CC}}{R_E+R_E'}=\frac{12}{3.300\,\mathrm{k}\,\Omega+2.481\,\mathrm{k}\,\Omega}=2.076\,\mathrm{mA}\,,V_{O,pp,max}\approx 2\left(V_{CC}\right. \tag{2.9}$$

The designed circuit has $I_{EQ}=2.085$ mA and $V_{CEQ}=5.119$ V, which is almost exactly the optimum ($I_{EQ}R_E'=5.173$ V). The most important parameters for the swing are therefore (1) the bias resistors R_1, R_2 (the Q point), (2) the emitter and load resistors R_E, R_L (the slope of the AC load line), (3) the supply voltage V_{CC} (the available range) and (4) $V_{CE(sat)}$. The effects were investigated by SPICE simulations in which R_2 and R_L were changed (Table 2.4.1, Figure 2.4.1); in each case, the DC values V_{CEQ} and I_{EQ} were found first, the two limits were calculated, and the largest output amplitude with THD ≤1 % was found by simulation.

Table 2.4.1 Effect of the bias resistor R_2 on the output swing of the common-collector amplifier (R_1 = 22 kΩ)

R_2 (kΩ)	V_{CEQ} SPICE (V)	I_{EQ} (mA)	Sat. limit (V)	Cut-off limit (V)	Load-line $V_{O,pp}$ (V)	SPICE $V_{O,pp}$, THD≤1% (V)
12.0	8.42	1.08	8.23	2.68	5.36	5.47
18.0	7.29	1.42	7.10	3.53	7.06	7.26
27.0	6.13	1.78	5.93	4.41	8.82	9.09
39.0	5.12	2.09	4.92	5.17	9.84	10.4
56.0	4.23	2.36	4.02	5.85	8.04	10.4
82.0	3.43	2.60	3.22	6.45	6.44	10.4
150	2.49	2.89	2.28	7.16	4.56	10.5

Table 2.4.2 Effect of the load resistor R_L on the output swing (R_1 = 22 kΩ, R_2 = 39 kΩ)

R_L (kΩ)	Sat. limit (V)	Cut-off limit (V)	Load-line $V_{O,pp}$ (V)	SPICE $V_{O,pp}$ (V)
1.00	4.92	1.60	3.20	3.06
2.20	4.92	2.75	5.50	5.55
4.70	4.92	4.04	8.08	8.28
10.0	4.92	5.17	9.84	10.4
22.0	4.92	5.98	9.84	11.3
47.0	4.92	6.43	9.84	11.7

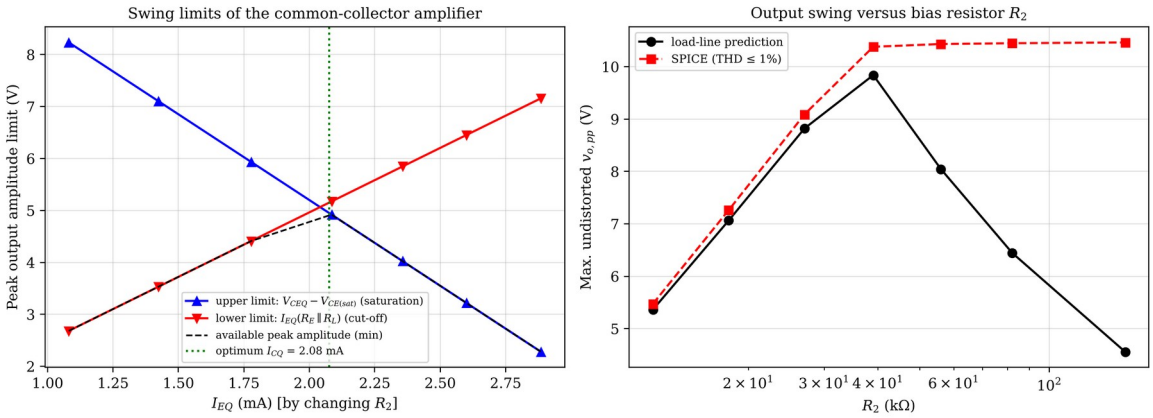


Figure 2.4.1 Swing limits and simulated swing of the common-collector amplifier versus the bias current (left) and R_2 (right).

The results show the following. (1) For a small bias current ($R_2 \leq 27$ kΩ), the swing is limited by cut-off ($I_{EQ} R_E'$) and grows in proportion to I_{EQ}; the load-line prediction and the simulation agree within 4%. (2) Around the optimum bias ($R_2 \approx 39$ kΩ), both limits are almost equal and the load-line swing is maximum (9.84 V). (3) For a larger bias current, the load line predicts a decrease of the swing since V_{CEQ} becomes small (saturation limit), but the simulation shows a plateau of about 10.5 V peak-to-peak: with a large signal, the peaks of the base current charge the coupling capacitor C_{C1} and lower the average base voltage (for $R_2 = 150$ kΩ and a 4 V input, the average base voltage falls from 10.1 V to 8.7 V), which moves the bias point towards the centre of the available range automatically. (4) A larger load resistor increases the cut-off limit ($I_{EQ} R_E'$) until the saturation limit (4.92 V) takes over; for $R_L \geq 10$ kΩ, the swing no longer improves in the load-line prediction, and the simulation gives 11.7 V peak-to-peak for $R_L = 47$ kΩ, close to the supply limit of 12 V. In summary, the swing is maximum when the Q point is at the middle of the AC load line, the load resistance is not small compared with R_E, and the supply voltage is as high as possible; V_{CEQ} must be kept above $V_{CE(sat)}$ plus the half swing, and V_{CE} must be monitored during the simulation to see on which side the clipping starts.

3 CONCLUSIONS

The comparison of the calculations and SPICE showed that the DC operating points agree within about 2% (V_{CEQ}: -1.5% for the common-emitter and +0.0% for the common-collector circuit), and that the voltage gains at 100 kHz agree within 0.1% (+0.0% and -0.0%) when the capacitor impedances are included in the calculation. The mid-band gain of the common-emitter amplifier with C_E ($|A_V| = 184$) is not reached at 100 kHz, since the 22 nF bypass capacitor has an impedance of 72 Ω at this frequency, which is larger than $r_e = 22.1\,\Omega$; the measured gain is 52.8, and the simulated maximum of the frequency response is 178 at 1585 kHz (-3.3% relative to the hand value) because the model parameters and the transistor capacitances differ from the ideal model. The input resistance with C_E at 100 kHz is smaller in SPICE (9.88 versus 10.7 kΩ) because of the Miller effect of the collector capacitance, which is not included in the hand analysis.

The largest undistorted output of the common-emitter amplifier with C_E is only 0.764 V peak-to-peak, which is limited by the exponential characteristic and not by clipping (the load-line value is 6.24 V); the emitter resistor increases the linear range by a factor of about 146 at the

cost of the gain (2.22 instead of 52.7). The emitter follower has a gain of 0.995, a high input resistance (13.6 kΩ), a low output resistance (12.4 Ω) and a large swing (9.84 V peak-to-peak by the load line), and its gain cannot be doubled. The swing is maximum when the Q point is at the middle of the AC load line, which the given design nearly satisfies.

4 REFERENCES

1. Fairchild Semiconductor. (2002). BC237/238/239 NPN epitaxial silicon transistor [Data sheet, Rev. A2]. Retrieved October 11, 2026, from https://wmsc.lcsc.com/wmsc/upload/file/pdf/v2/lcsc/2309151357_onsemi-BC237_C3201628.pdf
2. Sedra, A. S., & Smith, K. C. (2014). Microelectronic circuits (7th ed.). New York: Oxford University Press.
3. ngspice. (n.d.). ngspice user manual. Retrieved October 11, 2026, from https://ngspice.sourceforge.io/docs.html

5 APPENDICES

5.1 Appendix A: SPICE Model and Netlists

Code A.1 BJT model line used in the ngspice simulations (see Experiment 4 for the fitting of the parameters)

```
.model BC238A NPN(IS=7.7754e-14 BF=170 BR=1 RB=30 RC=1 CJE=8p CJC=3.5p TF=0.5n)
```

Netlist A.2 Common-emitter amplifier with C_E (AC analysis; the transient netlist differs only in the analysis command)

```
VCC vcc 0 DC 12
Vi in 0 DC 0 AC 1 SIN(0 0.001 100000)
Cc1 in b 22n
R1 vcc b 120k
R2 b 0 39k
RC vcc c 5.6k
Q1 c b e BC238A
RE e 0 1.8k
CE e 0 22n
Cc2 c o 2.2n
RL o 0 15k
.model BC238A NPN(IS=7.7754e-14 BF=170 BR=1 RB=30 RC=1 CJE=8p CJC=3.5p TF=0.5n)

.ac dec 60 10 100Meg
.end
```

Netlist A.3 Common-collector amplifier (AC analysis)

```
VCC vcc 0 DC 12
Vi in 0 DC 0 AC 1 SIN(0 0.001 100000)
Cc1 in b 22n
```

```
R1 vcc b 22000
R2 b 0 39000
Q1 vcc b e BC238A
RE e 0 3300
Cc2 e o 2.2n
RL o 0 10000
.model BC238A NPN(IS=7.7754e-14 BF=170 BR=1 RB=30 RC=1 CJE=8p CJC=3.5p TF=0.5n)

.ac dec 60 10 100Meg
.end
```